

# FACULTY OF ENGINEERING & TECHNOLOGY

UNIVERSITY OF LUCKNOW



**Lecture Notes**

**Subject Code: EE-302**

**Electrical Measurement & Measuring Instruments  
(Measurement of Power in AC Circuit)**

**By:**

**Dr. Gaurav Gupta  
Assistant Professor  
Deptt. Of EE**

# POWER MEASUREMENT IN A THREE PHASE CIRCUIT

*The active power in an AC circuit is measured using Wattmeter.*

*A wattmeter is a measuring instrument provided with two coils :*

- *a pressure coil (potential coil )*
- *a current coil*

Deflection of the pointer  $\propto V I \cos (\Phi)$  i.e, Active power

## **Methods of measuring the power:**

- One wattmeter method
- Two wattmeter method
- Three wattmeter method

## Blondel's Theorem –

*Number of meters required to measure total power in balanced three-phase system is given by*

$$\text{number meters} = \text{number wires} - 1$$

### Example

2 elements
3 elements

3 phase 3-wire delta system

2-meters

3 phase 4-wire wye system

3-meters


3 phase 3 wire wye system

2-meters

Meters can be integrated into single unit that displays total power. Each integral meter is called an **element**
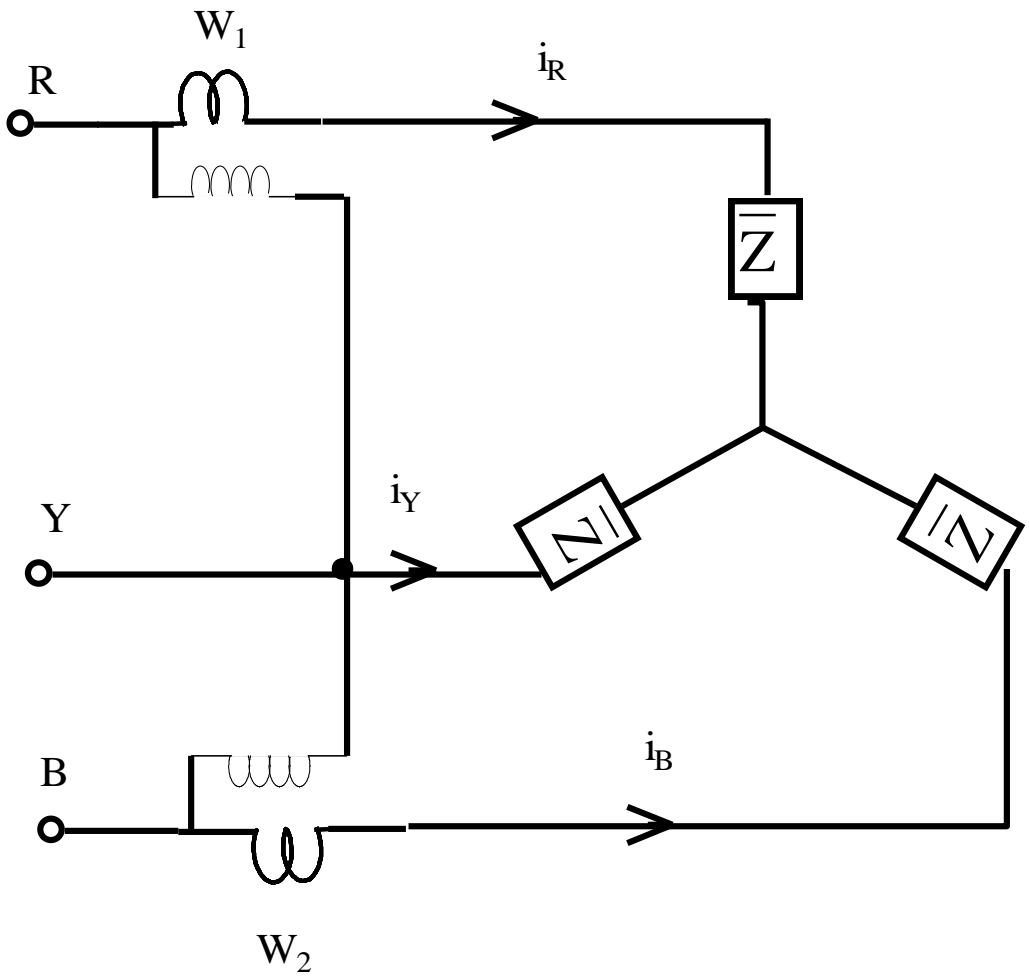
# Two wattmeter method



For balanced or unbalanced load (star or delta connected)



# TWO Wattmeter Method

Using RMS values: (balanced load only)

For Phase sequence RYB

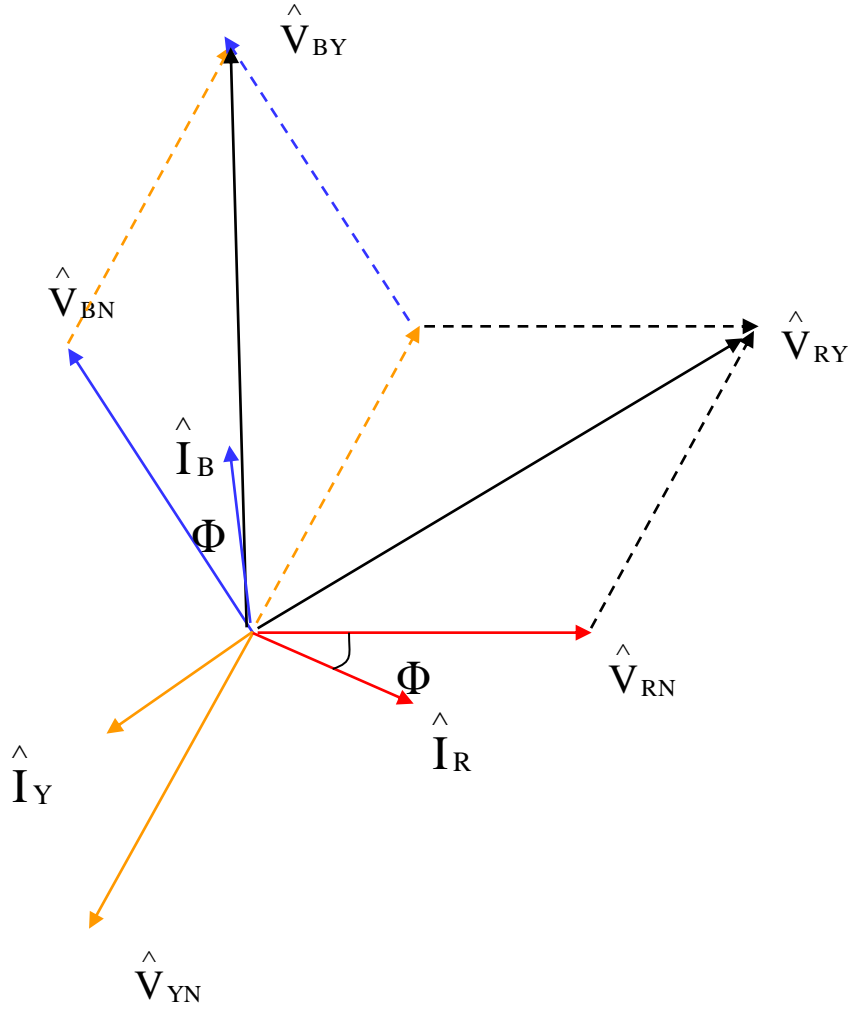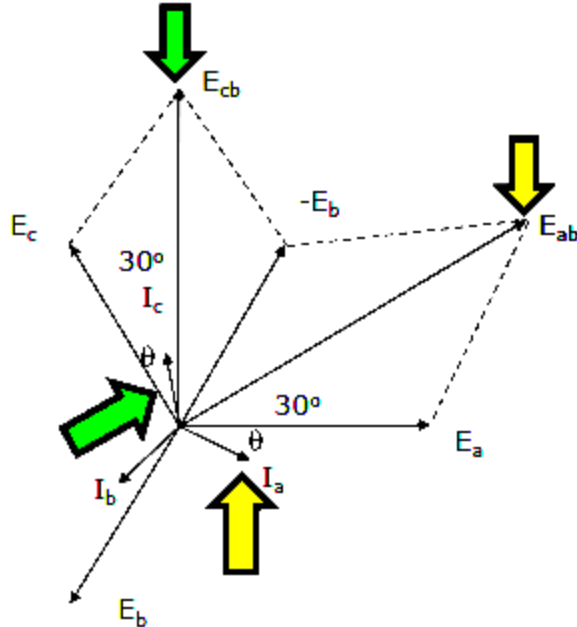

# TWO Wattmeter Method

- Supply voltage - symmetrical and balanced

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

For lagging power factor

- Power measured by  $W_1 = V_{RY} I_R \cos$  (angle between  $V_{RY}$  &  $I_R$ )

$$= V_L I_L \cos (30^\circ + \Phi)$$

- Power measured by  $W_2 = V_{BY} I_B \cos$  (angle between  $V_{BY}$  &  $I_B$ )

$$= V_L I_L \cos (30^\circ - \Phi)$$

$$W_1 + W_2 = V_L I_L [\cos (30^\circ + \Phi) + \cos (30^\circ - \Phi)]$$

$$= \sqrt{3} V_L I_L \cos \Phi = \text{Total active power}$$

# TWO Wattmeter Method

$$\begin{aligned}W_1 - W_2 &= V_L I_L [ \text{Cos} (30 + \Phi) - \text{Cos} (30 - \Phi) ] \\ &= -V_L I_L \text{Sin} \Phi\end{aligned}$$

$$\sqrt{3} \frac{W_2 - W_1}{W_2 + W_1} = \tan \phi$$

$$\phi = \tan^{-1} \left\{ \sqrt{3} \left( \frac{W_2 - W_1}{W_2 + W_1} \right) \right\}$$

$$\text{Cos} \phi = \text{Cos} \left[ \tan^{-1} \left\{ \sqrt{3} \left( \frac{W_2 - W_1}{W_2 + W_1} \right) \right\} \right]$$

# TWO Wattmeter Method

## Variation of Wattmeter readings with load power factor

$\Phi$ in degrees	PF	$W_1$	$W_2$	Remarks
0	1	$0.866 V_L I_L$	$0.866 V_L I_L$	Equal Readings
30	0.866	$0.5 V_L I_L$	$V_L I_L$	One wattmeter shows the double of the other
60	0.5	0	$0.866 V_L I_L$	One wattmeter shows ZERO
90	0	$-0.5 V_L I_L$	$0.5 V_L I_L$	One wattmeter shows the equal but opposite reading of the other

Disclaimer- This content is solely for the purpose of e-learning by students and any commercial use is not permitted. The author does not claim originality of the content and it is based on the references as listed.

References:

**Text Books:**

1. A.K. Sawhney, "Electrical & Electronic Measurement & Instrument", Dhanpat Rai & Sons, India
2. J.B. Gupta, "Electrical Measurements and Measuring Instruments", S.K. Kataria & Sons.

**Reference Books:**

1. W.D. Cooper, "Electronic Instrument and Measurement Technique", Prentice Hall International, India.
2. Forest K. Harries, "Electrical Measurement", Wiley Eastern Pvt. Ltd. India.
3. M.B. Stout, "Basic Electrical Measurement" Prentice hall of India, India.
4. E.W.Golding & F.C.Widdis, "Electrical Measurement & Measuring Instruments", A W Wheeler & Company Pvt. Ltd. India.